


A Report on **DIGITAL ASSIGNMENT**

Submitted in partial fulfilment of the course
EEE/INSTR F313: Analog and Digital VLSI design

By:

Parth Kalgaonkar
Pavni Jaiswal
Aditi Gupta

 2016A3PS0268P
2016A8PS0357P
2016A3PS0262P



Birla Institute of technology and Science, Pilani
October 2018

Contents

1	Problem Statement.....	3
1.1	Problem 35.....	3
2	Design of XOR gate.....	3
2.1	Schematic in Cadence	3
2.1.1	Specifications	3
2.2	Truth Table.....	5
2.3	Timing Diagram	6
2.4	Layout in Cadence.....	6
3	Radix-4 Booth multiplier	8
3.1	Pin description	8
3.1.1	Inputs	8
3.1.2	Outputs	9
3.2	Internal modules description.....	9
3.2.1	Sequence Counter.....	9
3.2.2	Accumulator.....	9
3.2.3	Bit extract.....	9
3.2.4	Partial product generator	9
3.2.5	Internal register	10
3.3	Verilog code	10
3.3.1	Top level module.....	10
3.3.2	Sequence counter	11
3.3.3	Accumulator.....	11
3.3.4	Bit Extract.....	12
3.3.5	Partial Product Generator.....	12
3.3.6	Internal Register.....	13
3.4	Simulation Results.....	13
3.5	Synthesis Results.....	14
3.5.1	Synthesized circuit	14
3.5.2	Synthesis reports.....	14

1 Problem Statement

1.1 Problem 35

(a) Design of a XOR gate

Design and simulate Transmission gate based 3-input XOR gate at 1GHz.

(b) Implement an eight-bit multiplier using Radix-4 Booth's algorithm using behavioral modeling.

2 Design of XOR gate

We have designed an Exclusive-OR gate using transmission gates only. The steps followed in achieving the same are as follows:

2.1 Schematic in Cadence

Two schematics have been designed for the implementation of the XOR gate using transmission gates. In the schematic, the transmission gates themselves have been designed using NMOS and PMOS.


2.1.1 Specifications

For transmission gate:


Each NMOS: $W/L = 20$

Each PMOS: $W/L = 60$

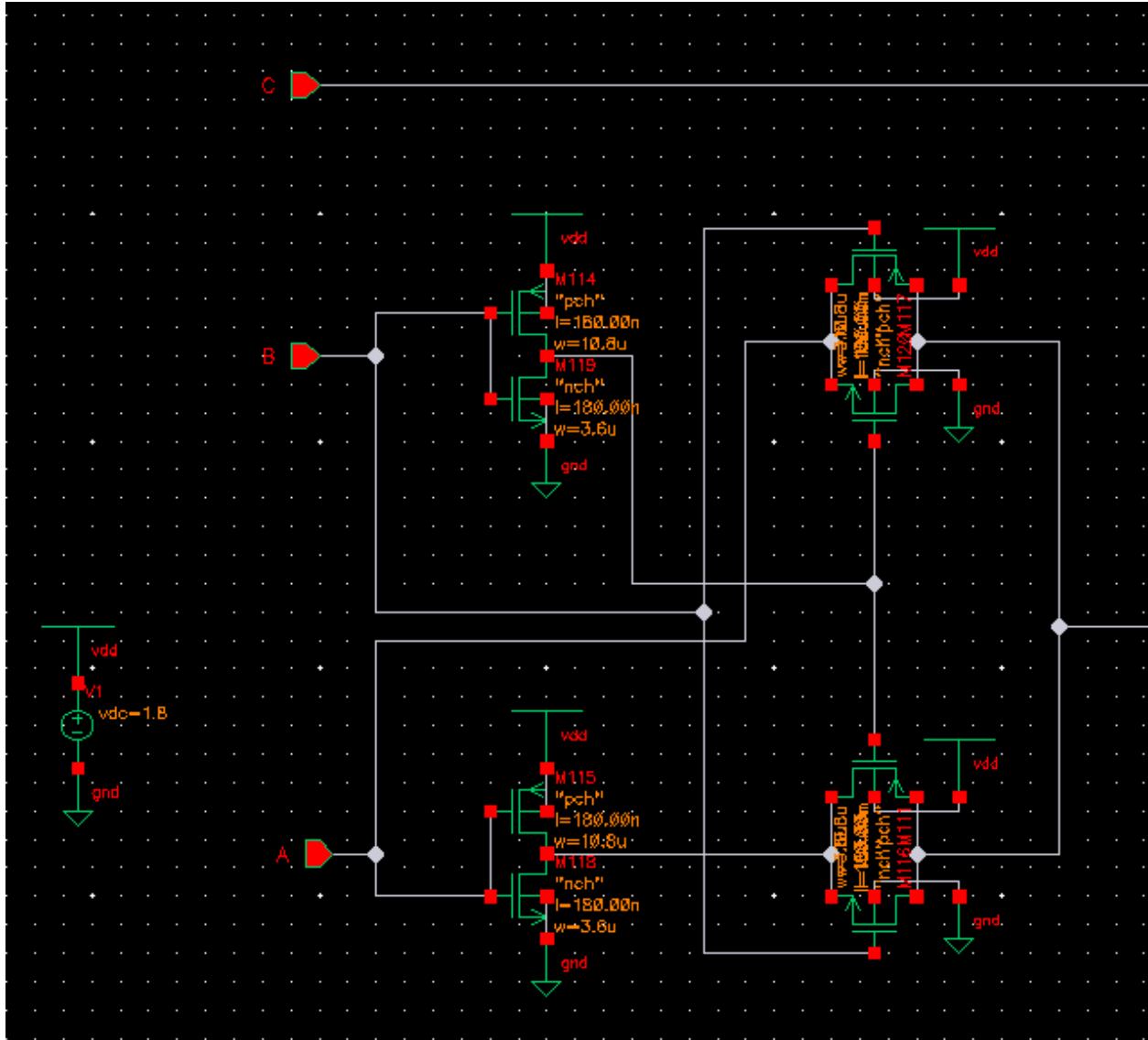For $L = 180$ nm technology, $W_{NMOS} = 3.6$ μm , $W_{PMOS} = 10.80$ μm



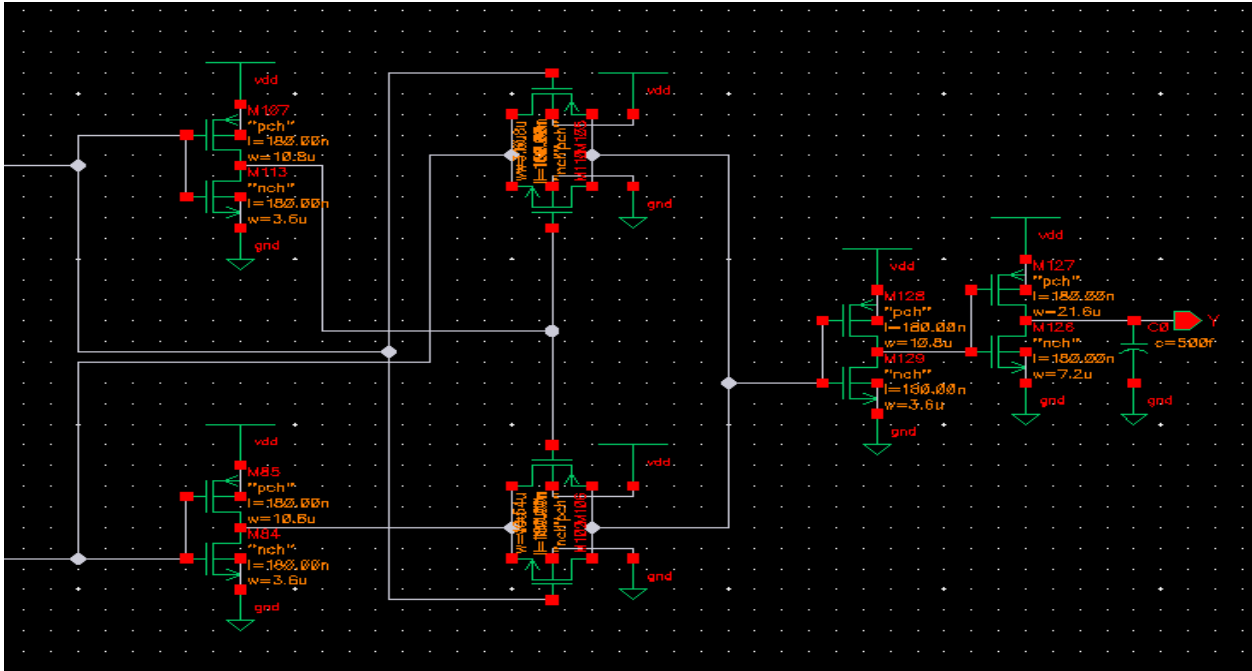Here, the two TGs take A and B as input and give $AB+A'B'$ as output.




The next two TGs take C and result of first two TGs, as input and give $AB'C' + A'BC' + A'B'C + ABC$ as output.

2.2 Truth Table

A	B	C	Output
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1


The schematic gives the final desired output as displayed in the timing diagram below:

2.3 Timing Diagram

 

 
2.4 Layout in Cadence

Cadence software has been used to design the layout corresponding to the circuit shown in the schematic above.



3 Radix-4 Booth multiplier

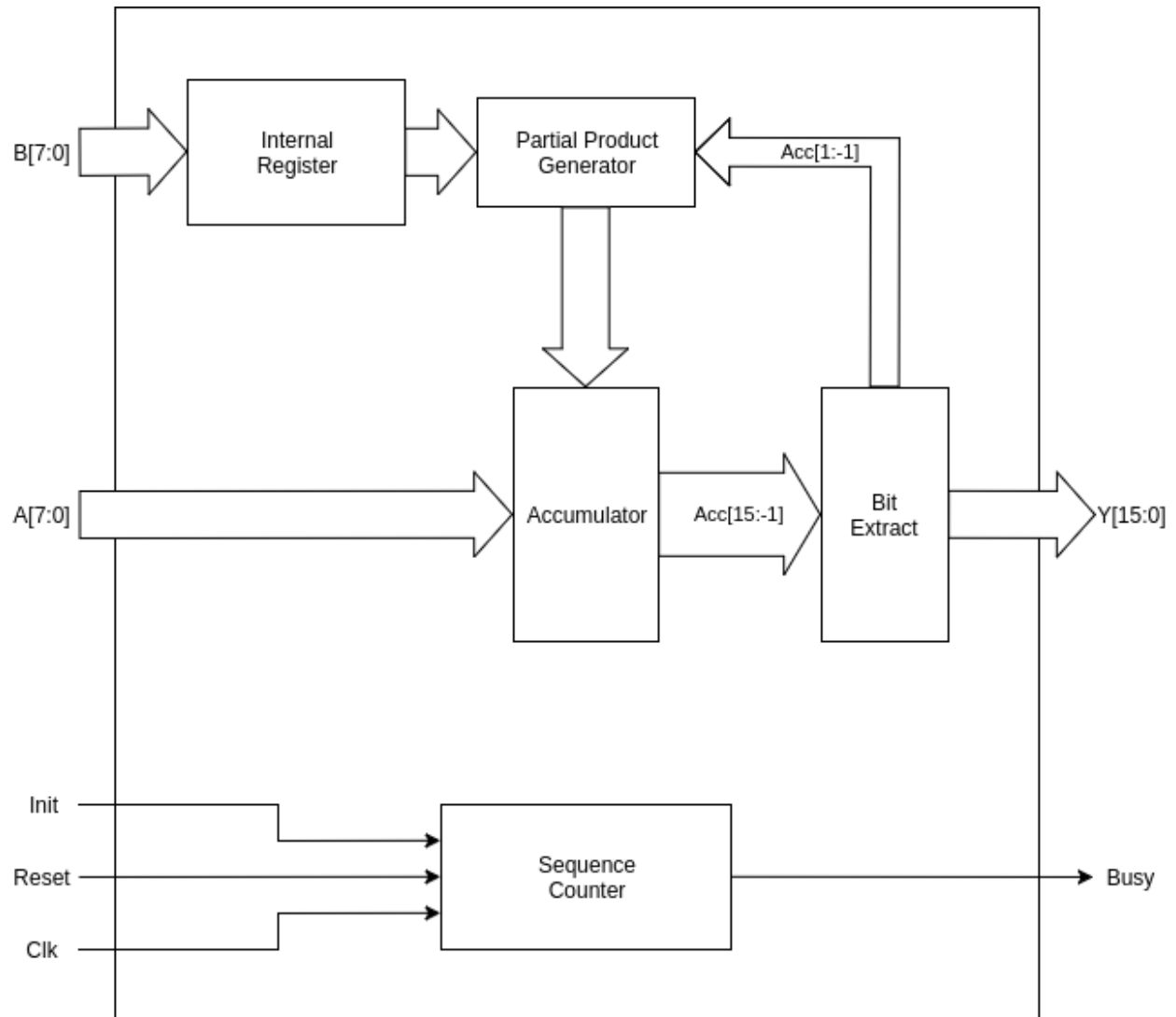We implemented booth multiplier using the following modules.



8-bit Radix-4 Booth Multiplier

3.1 Pin description

3.1.1 Inputs

- **$A[7:0]$** – This is the multiplier (or the first operand in multiplication).
- **$B[7:0]$** – The multiplicand (or second operand in multiplication).
- **Clk** – The input clock to the system for synchronization purposes. All system functions are positive edge triggered.

- **Reset** – System level active high reset signal. A logic **1** on this pin clears the sequence counter, **accumulator** and the internal registers. Logic **0** has no effect.
- **Init** – Start calculation. A logic **1** on this pin starts computation loads the internal register with the present value of **A** and the **accumulator** with the present value of **B**.

Note: Both **Reset** and **Init** are synchronous (changes are affected on the next rising edge of clock).

3.1.2 Outputs

- **Y[15:0]** – The result of multiplication. This value is only valid when the **busy** output is low. A reset clears the output.
- **Busy** – Logic **1** on this pin indicates that the multiplier is functioning to produce the correct output. This indicates that **sequence counter** is non-zero.

3.2 Internal modules description

3.2.1 Sequence Counter

This acts as the controller for the whole multiplier, generates internal signals for other modules, handles resets, start commands etc.

Contains a counter that counts down from four (the number of cycles req for 8-bit multiplication). As soon as count reaches 0, the **busy** signal is turned off indicating completion of operation.

3.2.2 Accumulator

Stores the intermediate result of adding partial products.

At every clock edge, the partial product (from the partial products generator) is added to the contents of the **accumulator** and the result is shifted (arithmetically) right by 2.

The implicit [-1] bit of the result is also stored in the **accumulator** and is used to find the partial products by the **partial product generator**.

3.2.3 Bit extract

The output of the **accumulator** is 17 bits (including the implicit [-1] bit). Of these, the most significant 16 are the actual bits of the result and the least significant three are used by the **partial product generator**.

Bit extract separates the two sets of bits, assigns the most significant 16 to the output and the least significant 3 as an input to the **partial products generator**.

3.2.4 Partial product generator

Based on the least significant three bits of the accumulator it generates the partial product for each iteration of the algorithm.

<i>Acc[1]</i>	<i>Acc[0]</i>	<i>Acc[-1]</i>	<i>Partial Product</i>
0	0	0	<i>O</i>
0	0	1	<i>B</i>
0	1	0	<i>B</i>
0	1	1	$2*B$
1	0	0	$-2*B$
1	0	1	$-B$
1	1	0	$-B$
1	1	1	<i>O</i>

Table 1: Partial Products in Radix-4 Booth

3.2.5 Internal register

This stores the value of the second operand **B** so that the device can be directly connected to system buses and the bus can function freely while the multiplier is busy.

3.3 Verilog code

3.3.1 Top level module

```

1 module mult_8bit(
2     input [7:0]a,
3     input [7:0]b,
4     input clk,
5     input reset,
6     input init,
7     output [15:0]y,
8     output busy
9 );
10
11 wire [2:0]x;
12 wire [7:0]m;
13 wire [16:0]z;
14 wire [7:0]c;
15
16 seq_count sc(
17     .clk(clk),
18     .reset(reset),
19     .init(init),
20     .busy(busy)
21 );
22
23 int_reg ir(
24     .clk(clk),
25     .init(init),
26     .reset(reset),

```

```

27     .a_in(a),
28     .a_out(c)
29 );
30
31 bit_extract be(
32     .a(z),
33     .x(x),
34     .y(y)
35 );
36
37 part_prod pp(
38     .x(x),
39     .a(c),
40     .m(m)
41 );
42
43 acc ac(
44     .q(b),
45     .m(m),
46     .clk(clk),
47     .init(init),
48     .busy(busy),
49     .reset(reset),
50     .a(z)
51 );
52 endmodule

```

3.3.2 Sequence counter

```

1 module seq_count(
2     input clk,
3     input reset,
4     input init,
5     output reg busy
6 );
7
8     reg [3:0]a;
9
10    always @(posedge clk) begin
11        if(reset) a <= 0;
12        else if (init) a <= 4;
13        else if(a>0) a <= a-1;
14    end
15
16    always @(*) begin
17        if(a==0) busy = 0;
18        else busy = 1;
19    end
20 endmodule

```

3.3.3 Accumulator

```

1 module acc(
2     input [7:0]q,

```

```

3   input [7:0]m,
4   input clk,
5   input init,
6   input busy,
7   input reset,
8   output reg [16:0]a
9 );
10
11  always @(posedge clk) begin
12      if(init) begin
13          a[8:1] <= q;
14      end
15      else if (reset) begin
16          a <= 0;
17      end
18      else if (busy) begin
19          a<=$signed(a+(m<<9))>>>2;
20      end
21  end
22 endmodule

```

3.3.4 Bit Extract

```

1 module bit_extract(
2     input [16:0]a,
3     output [2:0]x,
4     output [15:0]y
5 );
6
7     assign x = a[2:0];
8     assign y = a[16:1];
9
10 endmodule

```

3.3.5 Partial Product Generator

```

1 module part_prod(
2     input [2:0]x,
3     input [7:0]a,
4     output reg [7:0]m
5 );
6
7     always @(*) begin
8         case(x)
9             0: m = 0;
10            1: m = a;
11            2: m = a;
12            3: m = a<<1;
13            4: m = -(a<<1);
14            5: m = -a;
15            6: m = -a;
16            7: m = 0;
17        default: m = 0;
18    endcase

```

```

19     end
20 endmodule

```

3.3.6 Internal Register

```



1 module int_reg(
2     input clk,
3     input init,
4     input reset,
5     input [7:0]a_in,
6     output reg [7:0]a_out
7 );
8
9     always @(posedge clk) begin
10        if (reset) a_out<=0;
11        else if(init) a_out<=a_in;
12    end
13 endmodule

```

  3.4 Simulation Results

The design was compiled using Icarus Verilog, and the simulation waveform is displayed using gtkwave.

The simulation tests two input sets (-11x5) and (-11x-5) in succession. However, the results are shown separately for readability.




```

19     .Q (a[13]));
20 AO12RLXLP g1172(.A1 (n_31), .B1 (n_5), .B2 (a[15]), .O (n_34));
21 AO12RLXLP g1173(.A1 (n_31), .B1 (n_5), .B2 (a[14]), .O (n_33));
22 AO12RLXLP g1174(.A1 (n_31), .B1 (n_5), .B2 (a[16]), .O (n_32));
23 AOI112RLXLP g1175(.A1 (n_30), .B1 (n_6), .C1 (n_29), .C2 (n_3), .O
24     (n_31));
25 QDFCLRBRLX1 \a_reg[12] (.CK (clk), .D (n_27), .LD (n_7), .RB (n_0),
26     .Q (a[12]));
27 NR2RLXLP g1177(.I1 (n_3), .I2 (n_29), .O (n_30));
28 FA1RLX1 g1178(.A (a[15]), .B (m[6]), .CI (n_26), .S (n_28), .CO
29     (n_29));
30 QDFCLRBRLX1 \a_reg[11] (.CK (clk), .D (n_25), .LD (n_7), .RB (n_0),
31     .Q (a[11]));
32 FA1RLX1 g1180(.A (a[14]), .B (m[5]), .CI (n_24), .S (n_27), .CO
33     (n_26));
34 QDFCLRBRLX1 \a_reg[10] (.CK (clk), .D (n_23), .LD (n_7), .RB (n_0),
35     .Q (a[10]));
36 FA1RLX1 g1182(.A (a[13]), .B (m[4]), .CI (n_22), .S (n_25), .CO
37     (n_24));
38 QDFCLRBRLX1 \a_reg[9] (.CK (clk), .D (n_20), .LD (n_7), .RB (n_0), .Q
39     (a[9]));
40 FA1RLX1 g1184(.A (a[12]), .B (m[3]), .CI (n_19), .S (n_23), .CO
41     (n_22));
42 QDFFRXLX1 \a_reg[8] (.CK (clk), .D (n_21), .Q (a[8]));
43 AO222RLXLP g1186(.A1 (n_2), .A2 (q[7]), .B1 (n_17), .B2 (n_7), .C1
44     (n_4), .C2 (a[8]), .O (n_21));
45 FA1RLX1 g1187(.A (a[11]), .B (m[2]), .CI (n_16), .S (n_20), .CO
46     (n_19));
47 QDFFRXLX1 \a_reg[7] (.CK (clk), .D (n_18), .Q (a[7]));
48 QDFFRXLX1 \a_reg[1] (.CK (clk), .D (n_10), .Q (a[1]));
49 QDFFRXLX1 \a_reg[2] (.CK (clk), .D (n_15), .Q (a[2]));
50 QDFFRXLX1 \a_reg[3] (.CK (clk), .D (n_14), .Q (a[3]));
51 QDFFRXLX1 \a_reg[4] (.CK (clk), .D (n_13), .Q (a[4]));
52 QDFFRXLX1 \a_reg[5] (.CK (clk), .D (n_12), .Q (a[5]));
53 QDFFRXLX1 \a_reg[6] (.CK (clk), .D (n_11), .Q (a[6]));
54 QDFCLRBRLX1 \a_reg[0] (.CK (clk), .D (a[2]), .LD (n_7), .RB (n_0), .Q
55     (a[0]));
56 AO222RLXLP g1196(.A1 (n_2), .A2 (q[6]), .B1 (n_9), .B2 (n_7), .C1
57     (n_4), .C2 (a[7]), .O (n_18));
58 FA1RLX1 g1197(.A (a[10]), .B (n_8), .CI (m[1]), .S (n_17), .CO
59     (n_16));
60 AO222RLXLP g1198(.A1 (n_7), .A2 (a[4]), .B1 (n_4), .B2 (a[2]), .C1
61     (n_2), .C2 (q[1]), .O (n_15));
62 AO222RLXLP g1199(.A1 (n_7), .A2 (a[5]), .B1 (n_4), .B2 (a[3]), .C1
63     (n_2), .C2 (q[2]), .O (n_14));
64 AO222RLXLP g1200(.A1 (n_4), .A2 (a[4]), .B1 (n_7), .B2 (a[6]), .C1
65     (n_2), .C2 (q[3]), .O (n_13));
66 AO222RLXLP g1201(.A1 (n_7), .A2 (a[7]), .B1 (n_4), .B2 (a[5]), .C1
67     (n_2), .C2 (q[4]), .O (n_12));
68 AO222RLXLP g1202(.A1 (n_4), .A2 (a[6]), .B1 (n_7), .B2 (a[8]), .C1
69     (n_2), .C2 (q[5]), .O (n_11));
70 AO222RLXLP g1203(.A1 (n_7), .A2 (a[3]), .B1 (n_4), .B2 (a[1]), .C1
71     (n_2), .C2 (q[0]), .O (n_10));
72 HA1RLX1 g1204(.A (m[0]), .B (a[9]), .S (n_9), .C (n_8));
73 INVRLX1 g1205(.I (n_6), .O (n_7));
74 ND2RLXLP g1206(.I1 (n_1), .I2 (n_0), .O (n_6));
75 NR2RLXLP g1207(.I1 (reset), .I2 (n_1), .O (n_5));

```

```

76 NR3RLX1 g1208(.I1 (init), .I2 (reset), .I3 (busy), .O (n_4));
77 MAOI1RLXLP g1209(.A1 (m[7]), .A2 (a[16]), .B1 (a[16]), .B2 (m[7]), .O
78 (n_3));
79 AN2RLXLP g1210(.I1 (n_0), .I2 (init), .O (n_2));
80 AN2B1RLXLP g1211(.I1 (busy), .B1 (init), .O (n_1));
81 INVRLX1 g1213(.I (reset), .O (n_0));
82 endmodule
83
84 module int_reg(clk, init, reset, a_in, a_out);
85     input clk, init, reset;
86     input [7:0] a_in;
87     output [7:0] a_out;
88     wire clk, init, reset;
89     wire [7:0] a_in;
90     wire [7:0] a_out;
91     wire n_0, n_1, n_2, n_3, n_4, n_5, n_6, n_7;
92     QDFFRLX1 \a_out_reg[0] (.CK (clk), .D (n_1), .Q (a_out[0]));
93     QDFFRLX1 \a_out_reg[2] (.CK (clk), .D (n_0), .Q (a_out[2]));
94     QDFFRLX1 \a_out_reg[3] (.CK (clk), .D (n_7), .Q (a_out[3]));
95     QDFFRLX1 \a_out_reg[4] (.CK (clk), .D (n_6), .Q (a_out[4]));
96     QDFFRLX1 \a_out_reg[1] (.CK (clk), .D (n_4), .Q (a_out[1]));
97     QDFFRLX1 \a_out_reg[5] (.CK (clk), .D (n_5), .Q (a_out[5]));
98     QDFFRLX1 \a_out_reg[6] (.CK (clk), .D (n_3), .Q (a_out[6]));
99     QDFFRLX1 \a_out_reg[7] (.CK (clk), .D (n_2), .Q (a_out[7]));
100    MUXB2RLXLP g26(.S (init), .A (a_out[3]), .B (a_in[3]), .EB (reset),
101    .O (n_7));
102    MUXB2RLXLP g27(.S (init), .A (a_out[4]), .B (a_in[4]), .EB (reset),
103    .O (n_6));
104    MUXB2RLXLP g28(.S (init), .A (a_out[5]), .B (a_in[5]), .EB (reset),
105    .O (n_5));
106    MUXB2RLXLP g29(.S (init), .A (a_out[1]), .B (a_in[1]), .EB (reset),
107    .O (n_4));
108    MUXB2RLXLP g30(.S (init), .A (a_out[6]), .B (a_in[6]), .EB (reset),
109    .O (n_3));
110    MUXB2RLXLP g31(.S (init), .A (a_out[7]), .B (a_in[7]), .EB (reset),
111    .O (n_2));
112    MUXB2RLXLP g32(.S (init), .A (a_out[0]), .B (a_in[0]), .EB (reset),
113    .O (n_1));
114    MUXB2RLXLP g33(.S (init), .A (a_out[2]), .B (a_in[2]), .EB (reset),
115    .O (n_0));
116 endmodule
117
118 module part_prod(x, a, m);
119     input [2:0] x;
120     input [7:0] a;
121     output [7:0] m;
122     wire [2:0] x;
123     wire [7:0] a;
124     wire [7:0] m;
125     wire n_0, n_1, n_2, n_3, n_4, n_5, n_6, n_7;
126     wire n_8, n_9, n_10, n_12, n_13, n_14, n_15, n_16;
127     wire n_17, n_18, n_19, n_20, n_21, n_23, n_25, n_26;
128     wire n_28, n_29, n_31, n_32, n_34;
129     OAI122RLXLP g570(.A1 (n_19), .B1 (n_34), .B2 (n_12), .C1 (n_7), .C2
130     (n_32), .O (m[7]));
131     OAI122RLXLP g571(.A1 (n_16), .B1 (n_32), .B2 (n_12), .C1 (n_7), .C2
132     (n_29), .O (m[6]));

```



```

133 MAOI1RLXLP g572(.A1 (n_31), .A2 (a[7]), .B1 (a[7]), .B2 (n_31), .O
134 (n_34));
135 OAI122RLXLP g573(.A1 (n_15), .B1 (n_29), .B2 (n_12), .C1 (n_7), .C2
136 (n_26), .O (m[5]));
137 MAOI1RLXLP g574(.A1 (n_28), .A2 (a[6]), .B1 (a[6]), .B2 (n_28), .O
138 (n_32));
139 AN2B1RLXLP g575(.I1 (n_28), .B1 (a[6]), .O (n_31));
140 OAI122RLXLP g576(.A1 (n_14), .B1 (n_26), .B2 (n_12), .C1 (n_7), .C2
141 (n_23), .O (m[4]));
142 MAOI1RLXLP g577(.A1 (n_25), .A2 (a[5]), .B1 (a[5]), .B2 (n_25), .O
143 (n_29));
144 AN2B1RLXLP g578(.I1 (n_25), .B1 (a[5]), .O (n_28));
145 OAI122RLXLP g579(.A1 (n_18), .B1 (n_23), .B2 (n_12), .C1 (n_7), .C2
146 (n_13), .O (m[3]));
147 MAOI1RLXLP g580(.A1 (n_21), .A2 (a[4]), .B1 (a[4]), .B2 (n_21), .O
148 (n_26));
149 AN2B1RLXLP g581(.I1 (n_21), .B1 (a[4]), .O (n_25));
150 OAI122RLXLP g582(.A1 (n_17), .B1 (n_13), .B2 (n_12), .C1 (n_7), .C2
151 (n_3), .O (m[2]));
152 MAOI1RLXLP g583(.A1 (n_8), .A2 (a[3]), .B1 (a[3]), .B2 (n_8), .O
153 (n_23));
154 OAI122RLXLP g584(.A1 (n_20), .B1 (n_9), .B2 (n_0), .C1 (n_3), .C2
155 (n_12), .O (m[1]));
156 AN2B1RLXLP g585(.I1 (n_8), .B1 (a[3]), .O (n_21));
157 OAI12RLXLP g586(.A1 (a[0]), .B1 (n_6), .B2 (n_5), .O (n_20));
158 AOI22RLXLP g587(.A1 (n_10), .A2 (a[7]), .B1 (n_5), .B2 (a[6]), .O
159 (n_19));
160 AOI22RLXLP g588(.A1 (n_10), .A2 (a[3]), .B1 (n_5), .B2 (a[2]), .O
161 (n_18));
162 AOI22RLXLP g589(.A1 (n_10), .A2 (a[2]), .B1 (n_5), .B2 (a[1]), .O
163 (n_17));
164 AOI22RLXLP g590(.A1 (n_10), .A2 (a[6]), .B1 (n_5), .B2 (a[5]), .O
165 (n_16));
166 AOI22RLXLP g591(.A1 (n_10), .A2 (a[5]), .B1 (n_5), .B2 (a[4]), .O
167 (n_15));
168 AOI22RLXLP g592(.A1 (n_10), .A2 (a[4]), .B1 (n_5), .B2 (a[3]), .O
169 (n_14));
170 MAOI1RLXLP g593(.A1 (n_2), .A2 (a[2]), .B1 (a[2]), .B2 (n_2), .O
171 (n_13));
172 ND2RLXLP g594(.I1 (n_4), .I2 (x[2]), .O (n_12));
173 AN2RLXLP g595(.I1 (n_4), .I2 (a[0]), .O (m[0]));
174 INVRLX1 g596(.I (n_9), .O (n_10));
175 OR2B1RLXLP g597(.I1 (x[2]), .B1 (n_4), .O (n_9));
176 AN2B1RLXLP g598(.I1 (n_2), .B1 (a[2]), .O (n_8));
177 INVRLX1 g599(.I (n_6), .O (n_7));
178 AN3B2RLXLP g600(.I1 (x[2]), .B1 (x[0]), .B2 (x[1]), .O (n_6));
179 NR2RLXLP g601(.I1 (x[2]), .I2 (n_1), .O (n_5));
180 XOR2RLX1 g602(.I1 (x[0]), .I2 (x[1]), .O (n_4));
181 MXL2RLXLP g603(.S (a[0]), .A (a[1]), .B (n_0), .OB (n_3));
182 NR2RLXLP g604(.I1 (a[0]), .I2 (a[1]), .O (n_2));
183 ND2RLXLP g605(.I1 (x[0]), .I2 (x[1]), .O (n_1));
184 INVRLX1 g606(.I (a[1]), .O (n_0));
185 endmodule
186
187 module seq_count(clk, reset, init, busy);
188 input clk, reset, init;
189 output busy;

```

```

190 wire clk, reset, init;
191 wire busy;
192 wire \a[0] , \a[1] , \a[2] , n_0, n_1, n_2, n_4, n_5;
193 wire n_8, n_9, n_14, n_19;
194 OR3RLX1 g108(.I1 (\a[1] ), .I2 (\a[2] ), .I3 (\a[0] ), .O (busy));
195 INVRLX1 g109(.I (\a[0] ), .O (n_9));
196 QDFFRLX1 \a_reg[2] (.CK (clk), .D (n_8), .Q (\a[2] ));
197 MXL2RLXLP g222(.S (n_2), .A (reset), .B (n_14), .OB (n_8));
198 QDFCBRLX1 \a_reg[1] (.CK (clk), .D (n_5), .RB (n_2), .Q (\a[1] ));
199 QDFFRLX1 \a_reg[0] (.CK (clk), .D (n_19), .Q (\a[0] ));
200 MOAI1RLXLP g227(.A1 (n_0), .A2 (\a[1] ), .B1 (n_0), .B2 (\a[1] ), .O
201 (n_5));
202 MOAI1RLXLP g228(.A1 (n_1), .A2 (\a[2] ), .B1 (n_1), .B2 (\a[2] ), .O
203 (n_4));
204 NR2RLXLP g230(.I1 (init), .I2 (reset), .O (n_2));
205 OR2RLXLP g231(.I1 (\a[1] ), .I2 (\a[0] ), .O (n_1));
206 ND2RLXLP g232(.I1 (busy), .I2 (n_9), .O (n_0));
207 ND2RLX1 g2(.I1 (busy), .I2 (n_4), .O (n_14));
208 AN3RLX1 g237(.I1 (n_2), .I2 (busy), .I3 (n_9), .O (n_19));
209 endmodule
210
211 module mult_8bit(a, b, clk, reset, init, y, busy);
212 input [7:0] a, b;
213 input clk, reset, init;
214 output [15:0] y;
215 output busy;
216 wire [7:0] a, b;
217 wire clk, reset, init;
218 wire [15:0] y;
219 wire busy;
220 wire \c[0] , \c[1] , \c[2] , \c[3] , \c[4] , \c[5] , \c[6] , \c[7] ;
221 wire \m[0] , \m[1] , \m[2] , \m[3] , \m[4] , \m[5] , \m[6] , \m[7] ;
222 wire \z[0] ;
223 acc ac(.q (b), .m ({\m[7] , \m[6] , \m[5] , \m[4] , \m[3] , \m[2] ,
224 \m[1] , \m[0] }), .clk (clk), .init (init), .busy (busy), .reset
225 (reset), .a ({y, \z[0] }));
226 int_reg ir(.clk (clk), .init (init), .reset (reset), .a_in (a),
227 .a_out ({\c[7] , \c[6] , \c[5] , \c[4] , \c[3] , \c[2] , \c[1] ,
228 \c[0] }));
229 part_prod pp(.x ({y[1:0], \z[0] }), .a ({\c[7] , \c[6] , \c[5] ,
230 \c[4] , \c[3] , \c[2] , \c[1] , \c[0] }), .m ({\m[7] , \m[6] ,
231 \m[5] , \m[4] , \m[3] , \m[2] , \m[1] , \m[0] }));
232 seq_count sc(.clk (clk), .reset (reset), .init (init), .busy (busy));
233 endmodule

```

3.5.2.2 Summary report

```

===== Generated
by: Encounter(R) RTL Compiler v08.10-s116_1
Generated on: Sep 22 2018 07:27:03 PM
Module: mult_8bit
Technology library: fsd0k_a_generic_core_1d0vtc 2007Q2v1.3
Operating conditions: _nominal_ (balanced_tree)
Wireload mode: enclosed
Area mode: timing library
=====

```

Timing

Tracing clock networks.
Levelizing the circuit.
Computing delays.
Computing arrivals and requireds.

Warning : Possible timing problems have been detected in this design.
[TIM-11]

: The design is 'mult_8bit'.
: Use 'report timing -lint' for more information.

No paths found.

Area

Instance	Cells	Cell Area	Net Area	Wireload
mult_8bit	111	1282	0	enG5K (S)

(S) = wireload was automatically selected

Design Rule Check

Initializing DRC engine.

Max_transition design rule: no violations.

Max_capacitance design rule: no violations.

Max_fanout design rule: no violations.

3.5.2.3 Power report

=====
by: Encounter(R) RTL Compiler v08.10-s116_1 Generated

```

Generated on: Sep 22 2018 07:27:04 PM
Module: mult_8bit
Technology library: fsd0k_a_generic_core_1d0vtc 2007Q2v1.3
Operating conditions: _nominal_ (balanced_tree)
Wireload mode: enclosed
Area mode: timing library

```

=====

Instance	Cells	Leakage Power (nW)	Dynamic Power (nW)	Total Power (nW)
mult_8bit	111	3.218	21539.089	21542.307
ac	45	1.835	10342.762	10344.597
ir	16	0.551	4064.339	4064.890
pp	37	0.522	3647.662	3648.184

sc 13 0.311 1806.326 1806.637

3.5.2.4 Area utilization report

```
===== Generated
by:          Encounter(R) RTL Compiler v08.10-s116_1
Generated on: Sep 22 2018 07:27:03 PM
Module:      mult_8bit
Technology library: fsd0k_a_generic_core_1d0vtc 2007Q2v1.3
Operating conditions: _nominal_ (balanced_tree)
Wireload mode: enclosed
Area mode:    timing library
=====
```

Instance	Cells	Cell Area	Net Area	Wireload
mult_8bit	111	1282	0	enG5K (S)
ac	45	705	0	enG5K (S)
pp	37	249	0	enG5K (S)
ir	16	216	0	enG5K (S)
sc	13	112	0	enG5K (S)

(S) = wireload was automatically selected

3.5.2.5 Gates utilization

```
===== Generated
by:          Encounter(R) RTL Compiler v08.10-s116_1
Generated on: Sep 22 2018 07:27:04 PM
Module:      mult_8bit
Technology library: fsd0k_a_generic_core_1d0vtc 2007Q2v1.3
Operating conditions: _nominal_ (balanced_tree)
Wireload mode: enclosed
Area mode:    timing library
=====
```

Gate	Instances	Area	Library
AN2B1RLXLP	6	30.000	fsd0k_a_generic_core_1d0vtc
AN2RLXLP	2	10.000	fsd0k_a_generic_core_1d0vtc
AN3B2RLXLP	1	7.000	fsd0k_a_generic_core_1d0vtc
AN3RLX1	1	7.000	fsd0k_a_generic_core_1d0vtc
AO12RLXLP	3	21.000	fsd0k_a_generic_core_1d0vtc
AO222RLXLP	8	96.000	fsd0k_a_generic_core_1d0vtc
AOI112RLXLP	1	7.000	fsd0k_a_generic_core_1d0vtc
AOI22RLXLP	6	42.000	fsd0k_a_generic_core_1d0vtc
FA1RLX1	6	180.000	fsd0k_a_generic_core_1d0vtc
HA1RLX1	1	15.000	fsd0k_a_generic_core_1d0vtc
INVRX1	6	18.000	fsd0k_a_generic_core_1d0vtc
MAOI1RLXLP	7	63.000	fsd0k_a_generic_core_1d0vtc
MOAI1RLXLP	2	16.000	fsd0k_a_generic_core_1d0vtc

MUXB2RLXLP	8	80.000	fsd0k_a_generic_core_ld0vtc
MXL2RLXLP	2	14.000	fsd0k_a_generic_core_ld0vtc
ND2RLX1	1	4.000	fsd0k_a_generic_core_ld0vtc
ND2RLXLP	4	16.000	fsd0k_a_generic_core_ld0vtc
NR2RLXLP	5	20.000	fsd0k_a_generic_core_ld0vtc
NR3RLX1	1	6.000	fsd0k_a_generic_core_ld0vtc
OAI122RLXLP	7	63.000	fsd0k_a_generic_core_ld0vtc
OAI12RLXLP	1	6.000	fsd0k_a_generic_core_ld0vtc
OR2B1RLXLP	1	5.000	fsd0k_a_generic_core_ld0vtc
OR2RLXLP	1	5.000	fsd0k_a_generic_core_ld0vtc
OR3RLX1	1	7.000	fsd0k_a_generic_core_ld0vtc
QDFCLRBRXL1	6	156.000	fsd0k_a_generic_core_ld0vtc
QDFCRBRXL1	1	21.000	fsd0k_a_generic_core_ld0vtc
QDFFRLX1	21	357.000	fsd0k_a_generic_core_ld0vtc
XOR2RLX1	1	10.000	fsd0k_a_generic_core_ld0vtc

total	111	1282.000	

Type	Instances	Area	Area %

sequential	28	534.000	41.7
inverter	6	18.000	1.4
logic	77	730.000	56.9

total	111	1282.000	100.0